

## 0.1 Introduction

In this lab we use the CD4007 MOSFET transistor set to test NMOS and PMOS current-voltage relationships as seen in our previous simulations. With these I-V characteristics we can estimate transistor parameters such as  $W/L$  and  $V_t$ .