

0.1 Part 3

The i_D versus V_{SG} characteristics of the PMOS are as expected. Furthermore, increasing V_{SB} increases $|V_{tp}|$, which is in line with theory. Enough information is available to determine the $\frac{W}{L}$ ratios for the transistors, which turn out to be 2.019 for the NMOS and 1.740 for the PMOS. However, this is probably not terribly accurate since k'_n and k'_p are taken from the SPICE model. The threshold voltage is considerably different from the SPICE model, so there is reason to believe that the k parameters are as well. These parameters should be determined through further experimentation before making a definitive statement about the $\frac{W}{L}$ ratio of the transistor.

0.2 Part 4

The i_D versus V_{SD} characteristics for the PMOS are not at all consistent with intuition nor theory. One possibility is that the CD4007 chips have been damaged due to short circuits or other practical considerations, leading to the bizarre characteristics that make it act as a diode with a very high forward voltage. However, this is a difficult argument to make since the i_D versus V_{SG} characteristics are in tact. The measurement equipment or the circuit used to perform this analysis are likely the culprit.