

Figure 1: Circuit for Simulation 3

Simulation 3 is similar to Simulation 1 except that a PMOS is used instead of an NMOS.

 


Figure 2:  $I_D$  and  $\frac{\partial I_D}{\partial V_{SG}}$  versus  $V_{SG}$  for PMOS

Again, the transistor is in saturation when it exits cutoff because  $V_{SD} = 5V$  and  $V_{SG} < 5V$ , meaning  $V_{SG} - |V_t| < V_{SD}$ . For the PMOS, the definition  $g_m = \frac{\partial I_D}{\partial V_{SG}}$  shall be used.

Table 1: Simulation 3 Results			
Vsg [ V ]	gm from DC operating point simulation [ uA / V ]	gm from Graph [ uA / V ]	Percentage Error
2.25733	794.1	762.52	4.1%