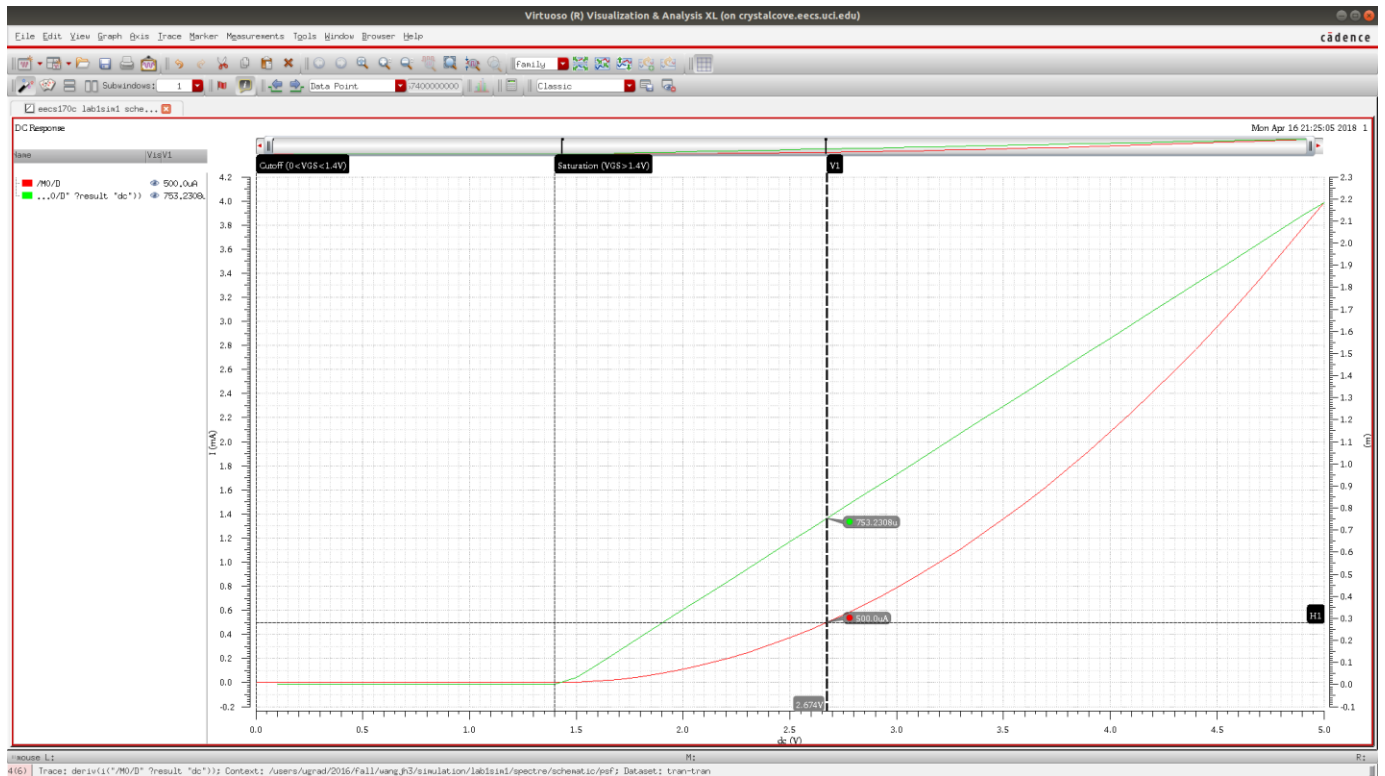


Sim 1

a)

Figure 1 – NMOS CS Amplifier I_D vs. V_{GS} Plot and Derivative

- b) When $I_D = 500 \mu A$, $V_{GS} = 2.674 V$. This V_{GS} value corresponds with $g_m = 753.231 \mu S$ from the derivative plot. The following is a hand calculation of transconductance.


$$g_m = \frac{2I_D}{V_{GS} - V_t} = \frac{2(500 \mu A)}{2.674 V - 1.4 V} = 784.929 \mu S$$

The hand calculated value of g_m above is reasonably close to the value found in the plot.


The value of g_m from the DC operating point simulation is **784 μS** , which is also close to the values above.

Sim 2


a)

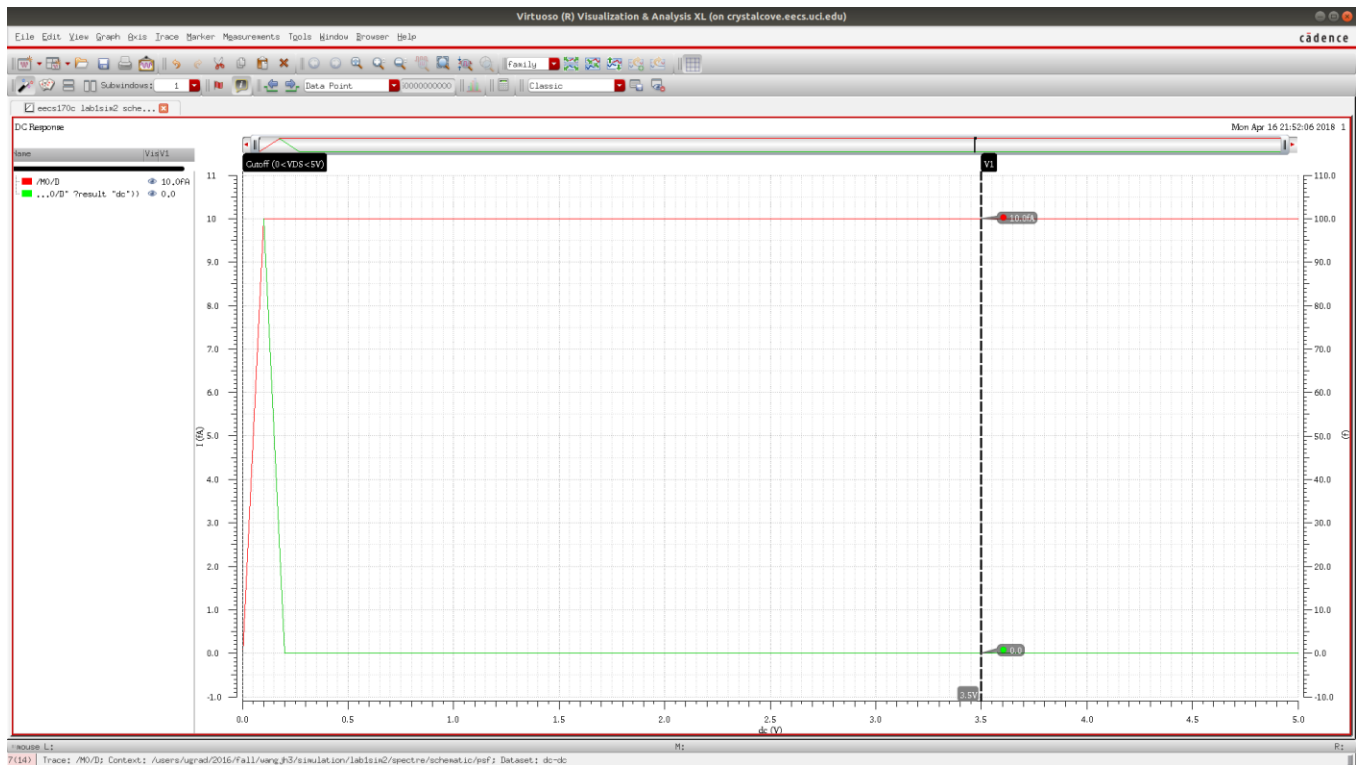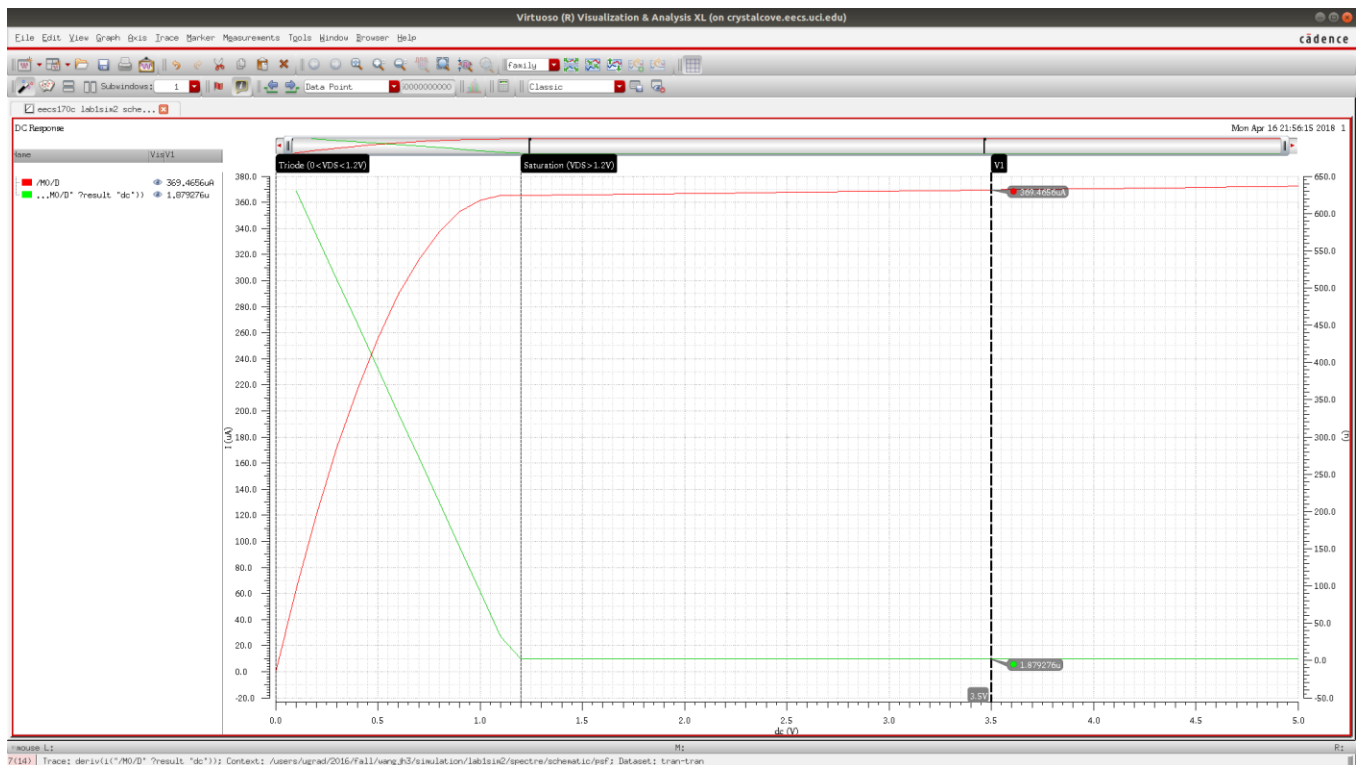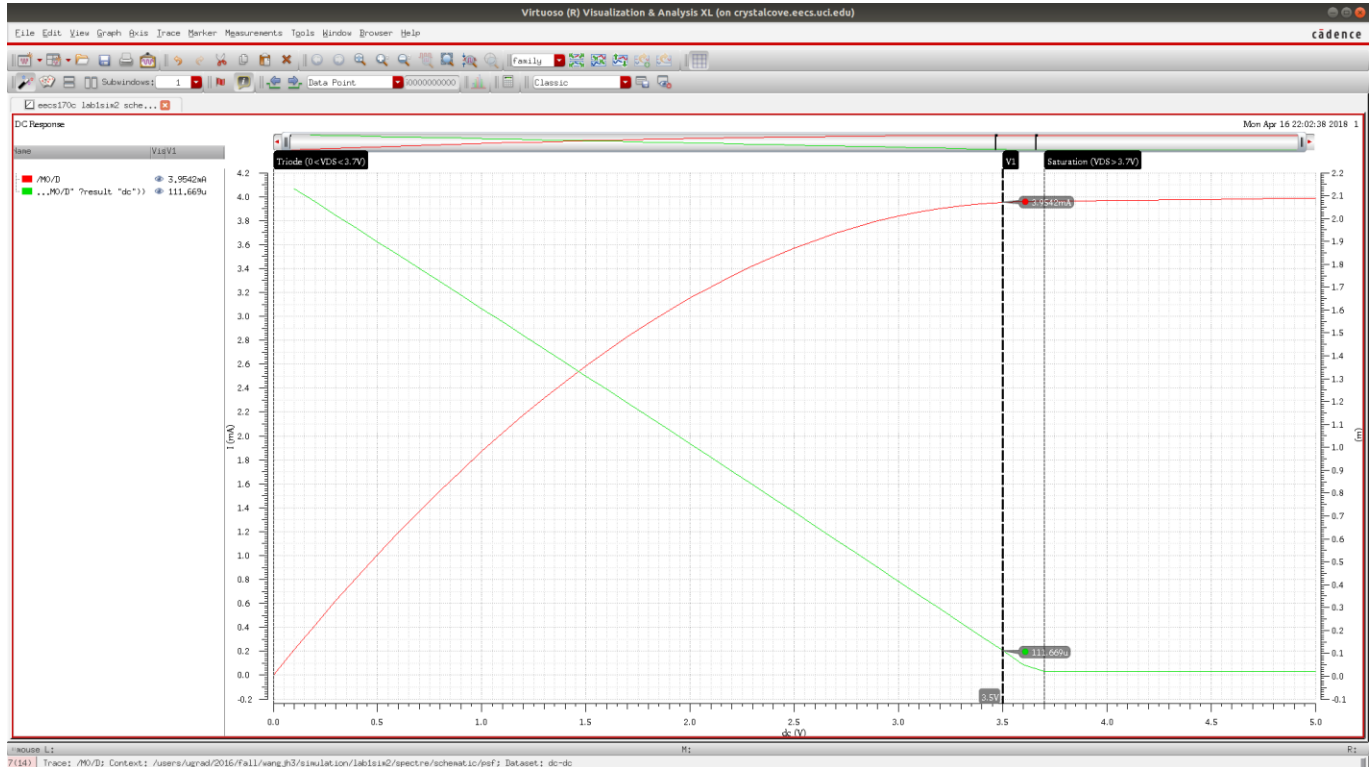Figure 2 - NMOS CS Amplifier I_D vs. V_{DS} Plot and Derivative, $V_{GS} = 0$ V

For the entire range of V_{DS} ($0 \text{ V} \leq V_{DS} \leq 5 \text{ V}$), the NMOS is in cutoff region for $V_{GS} = 0$ V.

Figure 3 - NMOS CS Amplifier I_D vs. V_{DS} Plot and Derivative, $V_{GS} = 2.5$ V

From $V_{DS} = 0$ to 1.2 V, the NMOS is in triode region. From $V_{DS} = 1.2$ to 5 V, the NMOS is in saturation region.

Figure 4 - NMOS CS Amplifier I_D vs. V_{DS} Plot and Derivative, $V_{GS} = 5$ V

From $V_{DS} = 0$ to 3.7 V, the NMOS is in triode region. From $V_{DS} = 3.7$ to 5 V, the NMOS is in saturation region.

- b) For $V_{GS} = 0$ V and $V_{DS} = 3.5$ V, g_{ds} is graphically found to be **0 uS**. This g_{ds} value produces the following λ .

$$g_{ds} = \frac{1}{r_o} = \lambda I_D \rightarrow \lambda = \frac{g_{ds}}{I_D} = \frac{0 \text{ S}}{10 \text{ fA}} = 0 \text{ V}^{-1}$$

For $V_{GS} = 2.5$ V and $V_{DS} = 3.5$ V, g_{ds} is graphically found to be **1.87276 uS**. This g_{ds} value produces the following λ .

$$g_{ds} = \frac{1}{r_o} = \lambda I_D \rightarrow \lambda = \frac{g_{ds}}{I_D} = \frac{1.87276 \text{ uS}}{369.466 \text{ uA}} = 5.069 \text{ m(V}^{-1}\text{)}$$

For $V_{GS} = 5$ V and $V_{DS} = 3.5$ V, g_{ds} is graphically found to be **111.67 uS**. This g_{ds} value produces the following λ .

$$g_{ds} = \frac{1}{r_o} = \lambda I_D \rightarrow \lambda = \frac{g_{ds}}{I_D} = \frac{111.67 \text{ uS}}{3954.2 \text{ uA}} = 28.240 \text{ m(V}^{-1}\text{)}$$


The valid λ value from the above calculations is **5.069 m(V⁻¹)** because the NMOS is operating in saturation.

From the DC operating point simulation, the g_{ds} values for $V_{GS} = 0$ V, 2.5 V, and 5 V are **0 uS**, **1.88 uS**, and **81.19 uS**, respectively. These values are close to the values found graphically except for the case in which $V_{GS} = 5$ V.

This inconsistency may be because 3.5 V is very close to the edge of triode and saturation in the $V_{GS} = 5$ V case.

Sim 3

a)

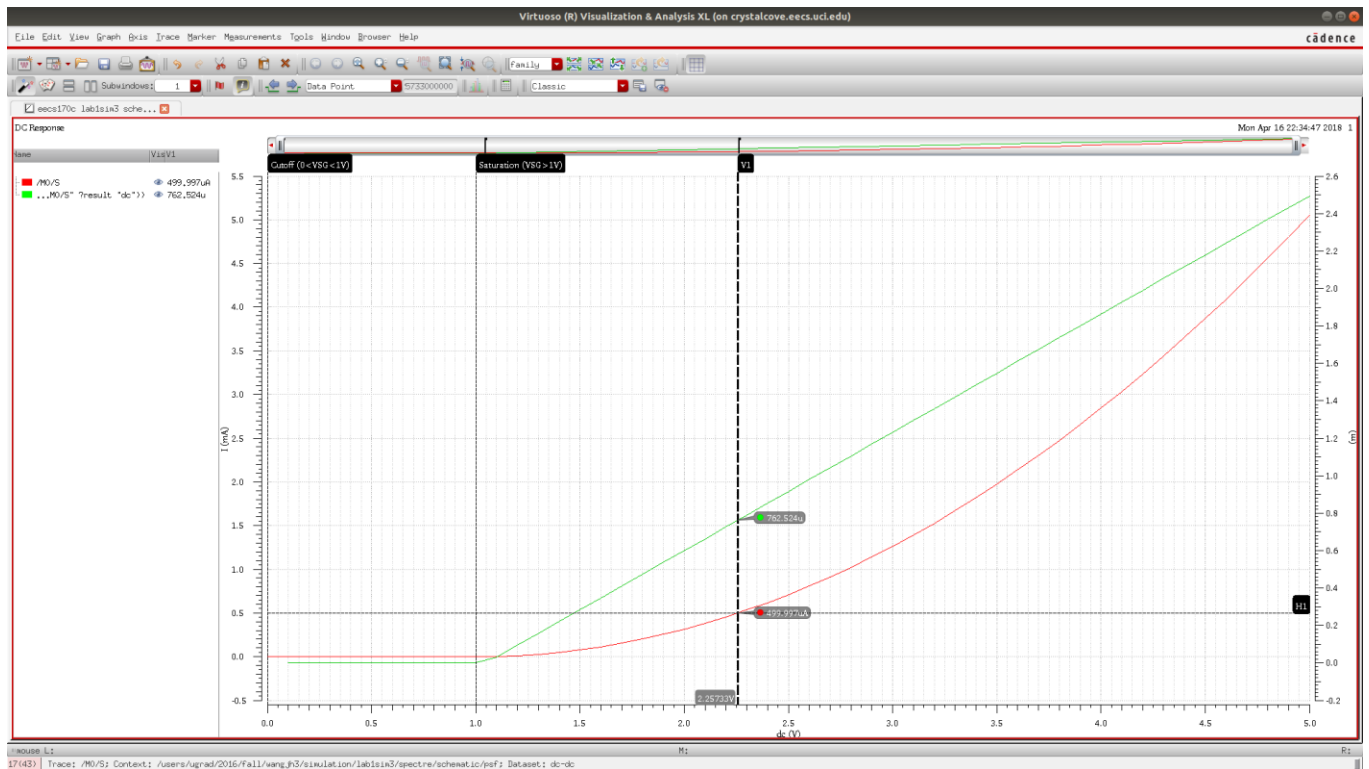Figure 5 – PMOS CS Amplifier I_D vs. V_{SG} Plot and Derivative

- b) When $I_D = 500 \mu\text{A}$, $V_{SG} = 2.25733 \text{ V}$. This V_{GS} value corresponds with $g_m = 762.524 \mu\text{S}$. The following is a hand calculation of transconductance.


$$g_m = \frac{2I_D}{V_{SG} - |V_t|} = \frac{2(500 \mu\text{A})}{2.25733 \text{ V} - 1.0 \text{ V}} = 795.336 \mu\text{S}$$

The hand calculated value of g_m above is reasonably close to the value found in the plot.


The value of g_m from the DC operating point simulation is **794.1 μS** , which is also close to the values above.

Sim 4


a)

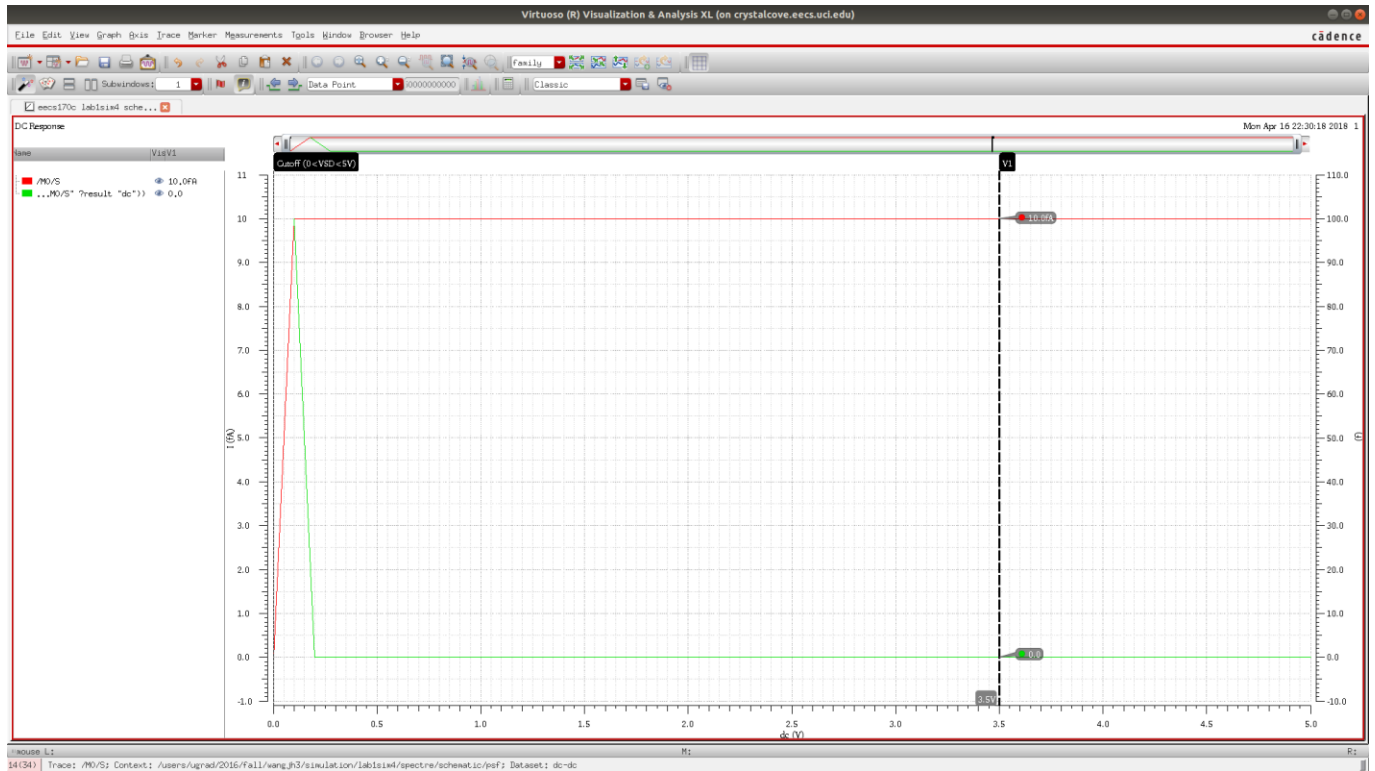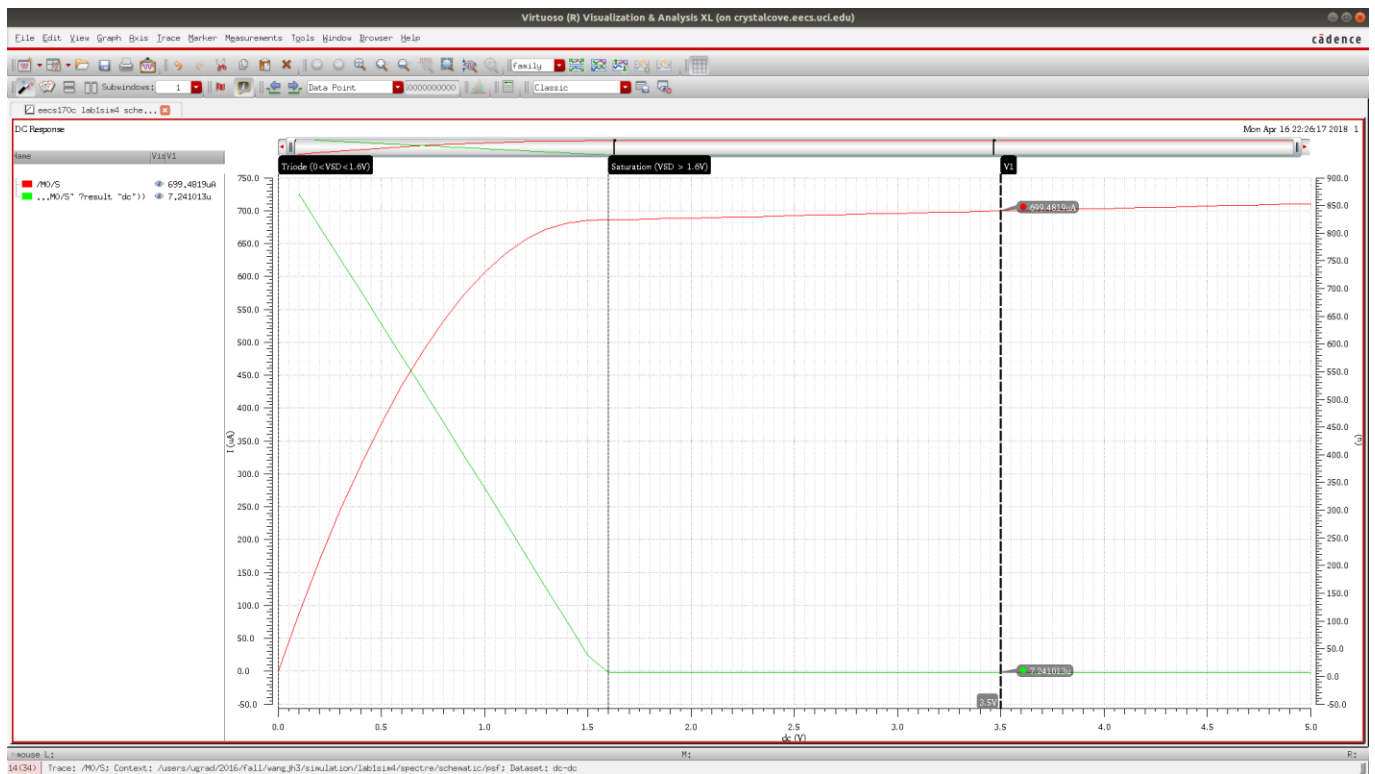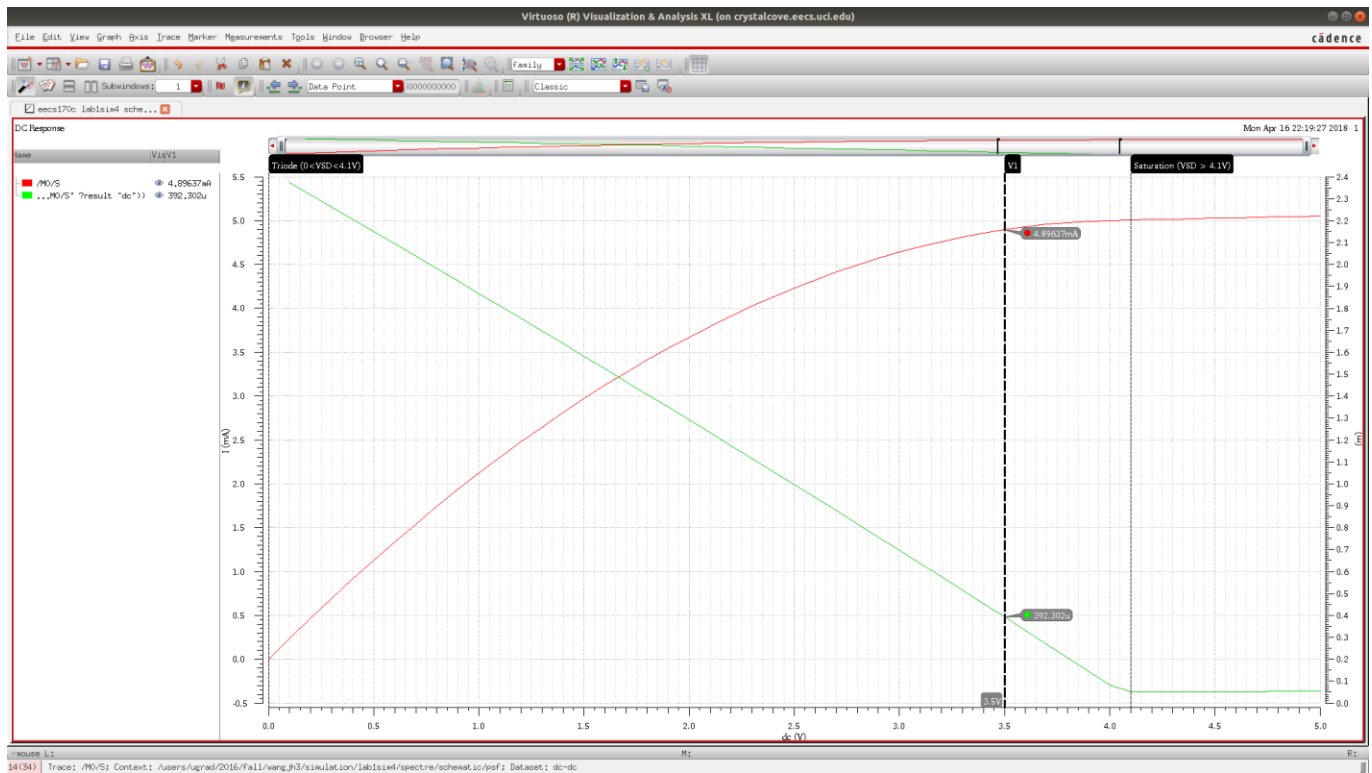Figure 6 - PMOS CS Amplifier I_D vs. V_{SD} Plot and Derivative, $V_{SG} = 0$ V

For the entire range of V_{SD} ($0 \text{ V} \leq V_{SD} \leq 5 \text{ V}$), the PMOS is in cutoff region for $V_{SG} = 0$ V.

Figure 7 - PMOS CS Amplifier I_D vs. V_{SD} Plot and Derivative, $V_{SG} = 2.5$ V

From $V_{SD} = 0$ to 1.6 V, the PMOS is in triode region. From $V_{SD} = 1.6$ to 5 V, the PMOS is in saturation region.

Figure 8 - PMOS CS Amplifier I_D vs. V_{SD} Plot and Derivative, $V_{SG} = 5$ V

From $V_{SD} = 0$ to 4.1 V, the PMOS is in triode region. From $V_{SD} = 4.1$ to 5 V, the PMOS is in saturation region.

- b) For $V_{SG} = 0$ V and $V_{SD} = 3.5$ V, g_{sd} is graphically found to be **0 uS**. This g_{ds} value produces the following λ .

$$g_{sd} = \frac{1}{r_o} = \lambda I_D \rightarrow \lambda = \frac{g_{ds}}{I_D} = \frac{0 \text{ S}}{10 \text{ fA}} = 0 \text{ V}^{-1}$$

For $V_{SG} = 2.5$ V and $V_{SD} = 3.5$ V, g_{sd} is graphically found to be **7.241013 uS**. This g_{ds} value produces the following λ .

$$g_{sd} = \frac{1}{r_o} = \lambda I_D \rightarrow \lambda = \frac{g_{ds}}{I_D} = \frac{7.241013 \text{ } \mu\text{S}}{699.4819 \text{ } \mu\text{A}} = 10.352 \text{ m}(\text{V}^{-1})$$

For $V_{SG} = 5$ V and $V_{SD} = 3.5$ V, g_{sd} is graphically found to be **392.302 uS**. This g_{ds} value produces the following λ .

$$g_{sd} = \frac{1}{r_o} = \lambda I_D \rightarrow \lambda = \frac{g_{ds}}{I_D} = \frac{392.302 \text{ } \mu\text{S}}{4896.37 \text{ } \mu\text{A}} = 80.121 \text{ m}(\text{V}^{-1})$$

The valid λ value from the above calculations is **10.352 m(V⁻¹)** because the PMOS is operating in saturation.

From the DC operating point simulation, the g_{ds} values for $V_{GS} = 0$ V, 2.5 V, and 5 V are **0 uS**, **7.249 uS**, and **361.6 uS**, respectively. These values are close to the values found graphically.