



Figure 1: Simulation 2 Sweep -  $V_{out,dm}$  versus  $V_{in,dm}$

Table (1) contains the ranges of input and output differential-mode values for which the transistors are biased in saturation.

Table 1: Conditions for All Transistors to be in Saturation

	Maximum [V]	Minimum [V]
DM Output Voltage	3.8794	-3.8957
DM Input Voltage	0.29189	-0.30875

The differential-mode gain can be acquired by computing the slope near  $V_{in,dm} = 0V$ . Table (2) contains these values. The theoretical prediction is very close to the simulation result.

Table 2: Simulation versus Theoretical Differential-Mode Gain

Theoretical Calculation [V/V]	Simulation Result [V/V]	Error
20.01	20.03	0.09%