

Figure 1: Circuit 4

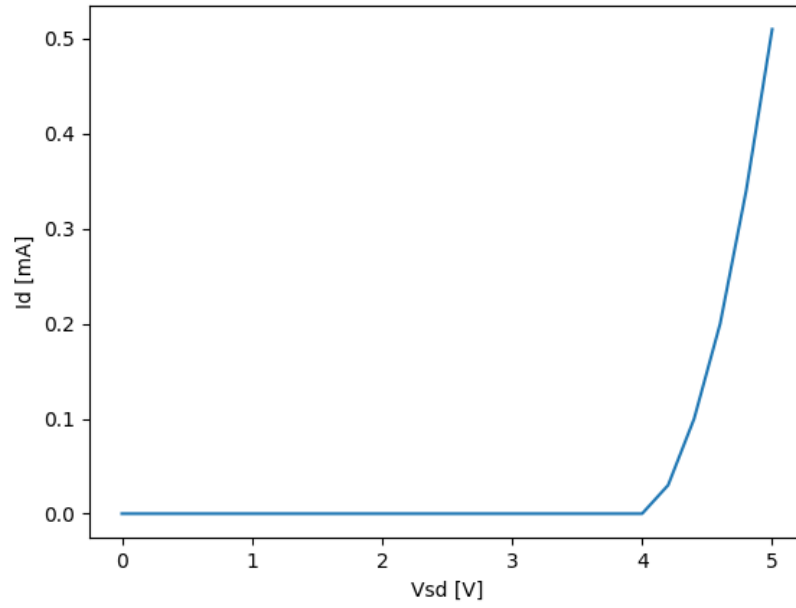


Figure 2:  $i_D$  versus  $V_{SD}$  for PMOS with  $V_{SG} = 2.5V$

One would hope to acquire similar results in figure (2) for the PMOS as are obtained for the NMOS. However, the results are drastically different. Reliable data for the  $V_{GS} = 5V$  case could not be acquired.